

Current in a RC Circuit The equation governing the amount of current I (in amperes) after time t (in microseconds) in a single RC circuit consisting of a resistance R (in ohms), a capacitance C (in microfarads), and an electromotive force E (in volts) is¹

$$I = \frac{E}{R}e^{-t/(RC)}$$

- (a) If $E = 120$ volts, $R = 2000$ ohms, and $C = 1.0$ microfarad, how much current I_1 is flowing initially ($t = 0$)? After 1000 microseconds? After 3000 microseconds?

We substitute into the given function.

$$I(t) = \frac{120}{2000}e^{-t/(2000 \cdot 1.0)}$$

$$I(0) = \frac{120}{2000}e^{-0/(2000 \cdot 1.0)}$$

$$I(0) = 0.06$$

Thus, the initial current at time $t = 0$ microseconds is 0.06 amperes.

$$I(t) = \frac{120}{2000}e^{-t/(2000 \cdot 1.0)}$$

$$I(1000) = \frac{120}{2000}e^{-1000/(2000 \cdot 1.0)}$$

$$I(1000) \approx 0.036$$

Thus, the current at time $t = 1000$ microseconds is 0.036 amperes.

$$I(t) = \frac{120}{2000}e^{-t/(2000 \cdot 1.0)}$$

$$I(3000) = \frac{120}{2000}e^{-3000/(2000 \cdot 1.0)}$$

$$I(3000) \approx 0.013$$

Thus, the current at time $t = 3000$ microseconds is 0.013 amperes.


- (b) What is the maximum current?

We graph the function $I(t) = \frac{120}{2000}e^{-t/(2000 \cdot 1.0)}$ on our graphing calculator. Let's use the domain $0 \leq t \leq 10000$ since the function seems to be decreasing, based on our work from part (a).

Thus the maximum current of 0.06 amperes occurs at $t = 0$ microseconds.

- (c) Graph the function $I = I_1(t)$, measuring I along the y -axis and t along the x -axis.

See graph at right.

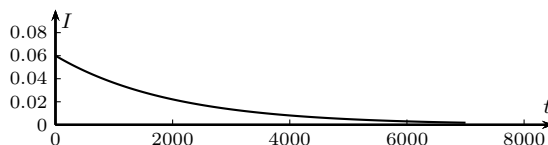

¹Sullivan, *Precalculus: Enhanced with Graphing Utilities*, p. 287, #114.